

CPE 301 - MICROPROCESSOR SYSTEM DESIGN  
Fall 2013

HOMEWORK No. 03 - DUE (beginning of class) September 17

NOTE: These problems are adapted from chapter 12 of *Digital Logic and Computer Design* by Morris Mano (Mano **Book2** Chapter 12 on WebCampus). There is also an additional memory design reference (Mano **Book1** Chapter 7 on WebCampus) which is from an earlier version of your CPE 201 textbook.

1.
  - (a) How many 128 X 8 RAM chips are needed to provide a memory capacity of 2048 bytes?
  - (b) How many lines of the address bus must be used to access 2048 bytes of memory? How many of these lines will be common to all chips?
  - (c) How many lines must be decoded for chip select? Specify the size of the decoders.
  
2. A microprocessor uses RAM chips of 1024 X 1 capacity.
  - (a) How many chips are needed and how should their address lines be connected to provide a memory capacity of 1024 bytes?
  - (b) How many chips are needed to provide a memory capacity of 16K bytes? Explain in words how the chips are to be connected to the address bus.
  
3. A ROM chip of 1024 X 8 bits has four select inputs and operates from a 5-volt power supply. How many pins are needed for the IC package? Draw a block diagram and label all input and output terminals in the ROM.
  
4. Extend the memory system of Fig. 12-13 to 4096 bytes of RAM and 4096 bytes of ROM. List the memory-address map and indicate what size decoders are needed.
  
5. A microprocessor employs RAM chips of 256 X 8 and ROM chips of 1024 X 8. The microcomputer system needs 2K bytes of RAM, 4K bytes of ROM, and four interface units, each with four registers. A memory-mapped I/O configuration is used. The two highest-order bits of the address bus are assigned 00 for RAM, 01 for ROM, and 10 for interface registers.
  - (a) How many RAM and ROM chips are needed?
  - (b) Draw a memory-address map for the system.
  - (c) Give the address range in hexadecimal for RAM, ROM, and interface.
  
6. An 8-bit microprocessor has a 16-bit address bus. The first 15 lines of the address are used to select a bank of 32K bytes of memory. The high-order bit of the address is used to select a register which receives the contents of the data bus. Explain how this configuration can be used to extend the memory capacity of the system to 8 banks of 32K bytes each, for a total of 256K bytes of memory.